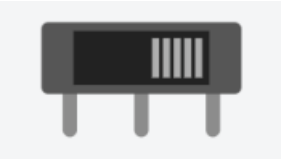
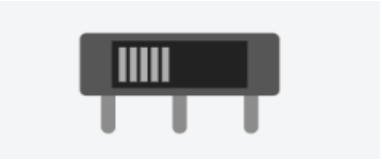
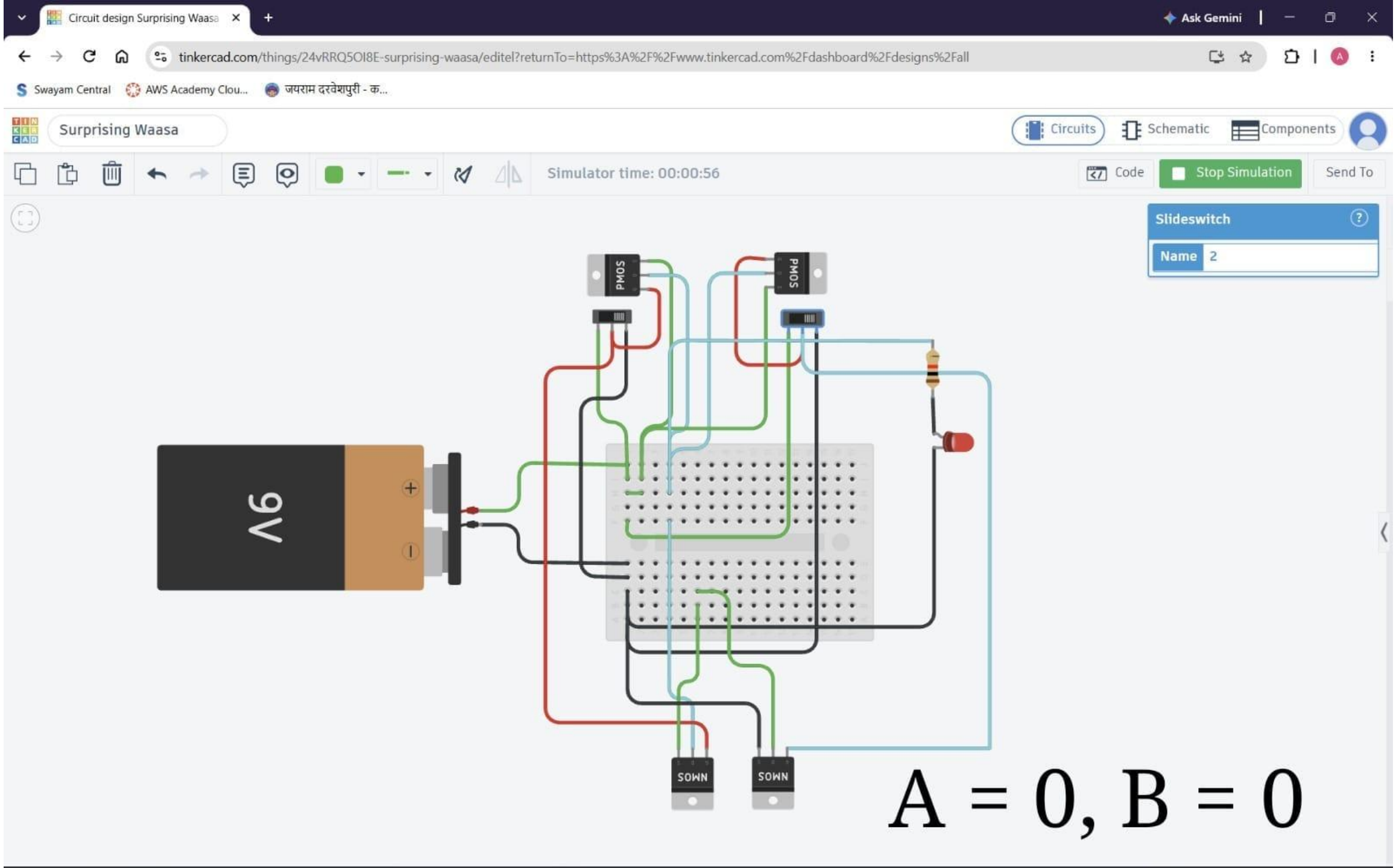
In the simulation, given below illustrates the orientation of the slide switch

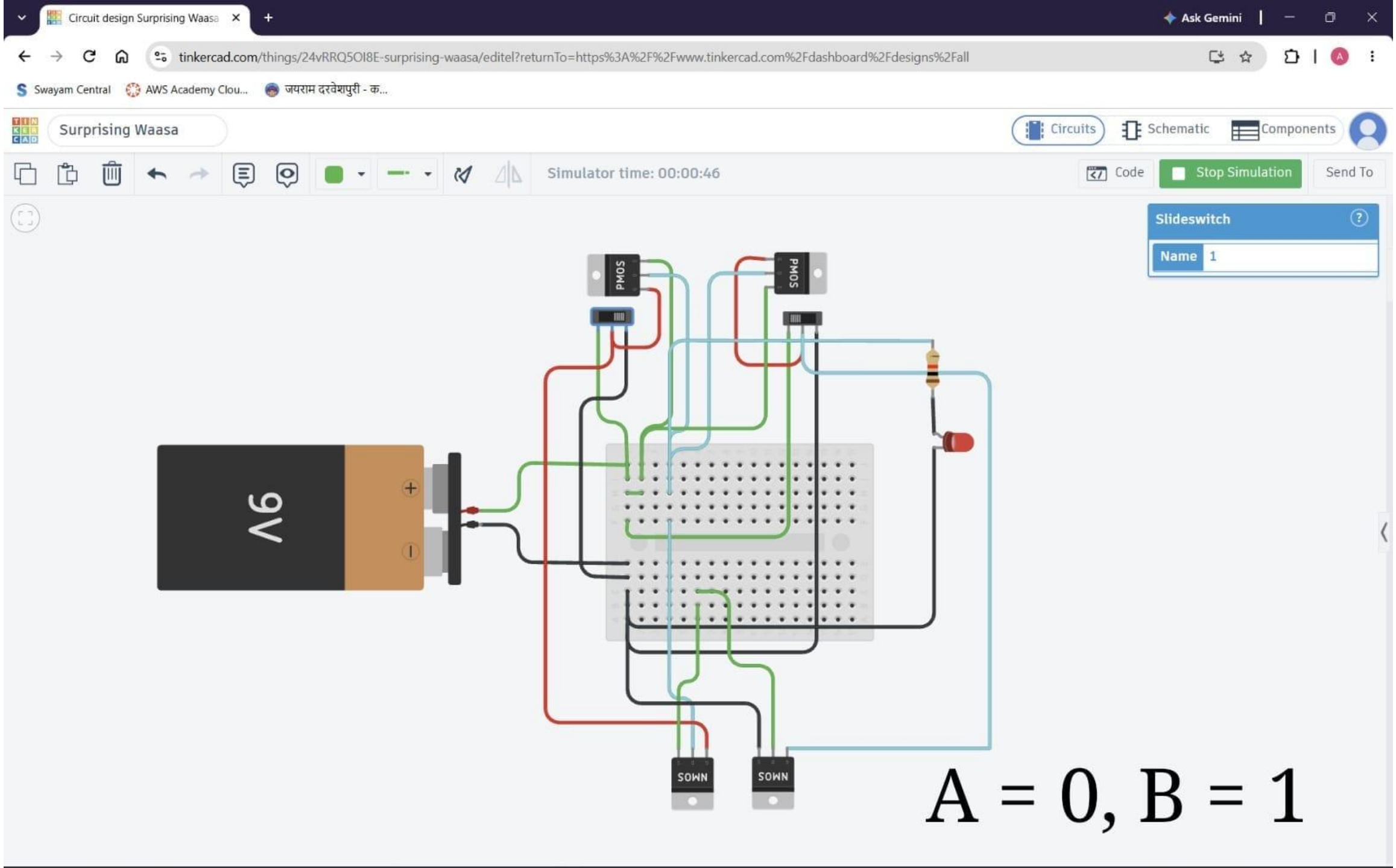


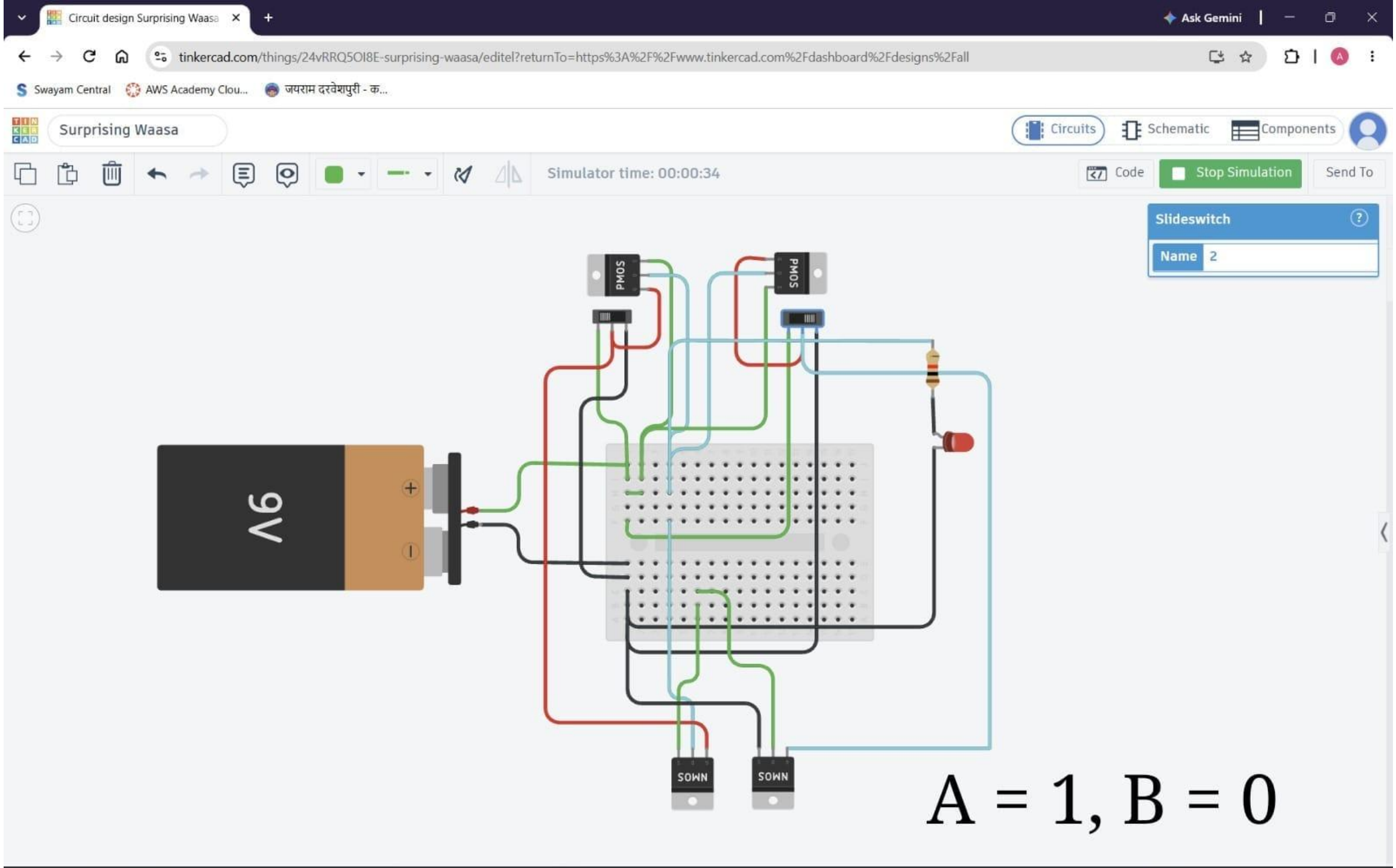
Switch OFF

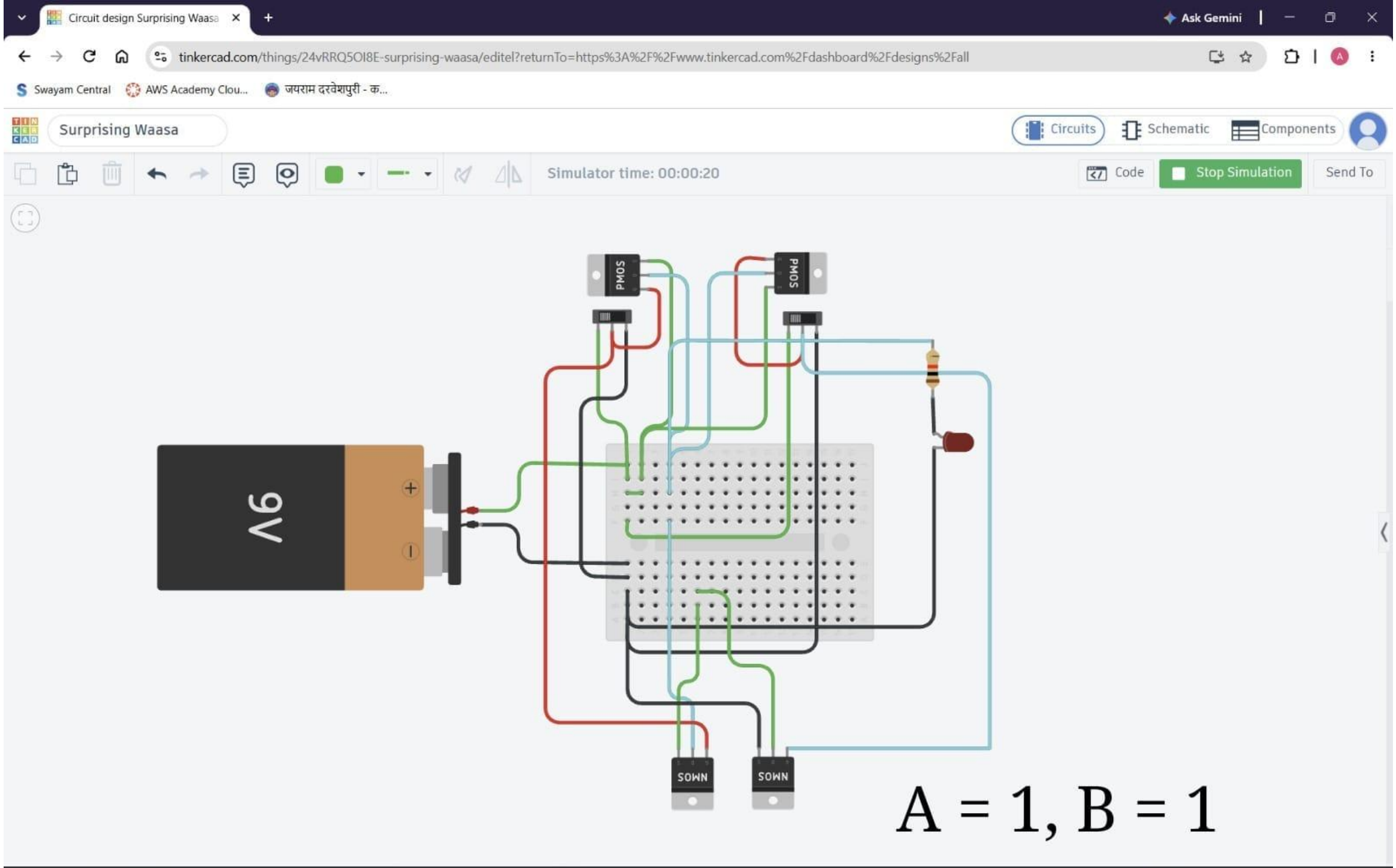


Switch ON


Circuit design Surprising Waasa
Ask Gemini
tinkercad.com/things/24vRRQ5OI8E-surprising-waasa/editel?returnTo=https%3A%2F%2Fwww.tinkercad.com%2Fdashboard%2Fdesigns%2Fall
Swayam Central
AWS Academy Clou...
जयराम दरवेशपुरी - क...
Surprising Waasa
Circuits
Schematic
Components
Simulator time: 00:00:56
Code
Stop Simulation
Send To
Slideswitch
Name 2
PMOS
PMOS
9V
SOWN
SOWN
A = 0, B = 0


Circuit design Surprising Waasa
Ask Gemini
tinkercad.com/things/24vRRQ5OI8E-surprising-waasa/editel?returnTo=https%3A%2F%2Fwww.tinkercad.com%2Fdashboard%2Fdesigns%2Fall
Swayam Central
AWS Academy Clou...
जयराम दरवेशपुरी - क...
Surprising Waasa
Circuits
Schematic
Components
Simulator time: 00:00:46
Code
Stop Simulation
Send To
Slideswitch
Name 1
PMOS
PMOS
9V
SOWN
SOWN
A = 0, B = 1


Circuit design Surprising Waasa
Ask Gemini
tinkercad.com/things/24vRRQ5OI8E-surprising-waasa/editel?returnTo=https%3A%2F%2Fwww.tinkercad.com%2Fdashboard%2Fdesigns%2Fall
Swayam Central
AWS Academy Clou...
जयराम दरवेशपुरी - क...
Surprising Waasa
Circuits
Schematic
Components
Simulator time: 00:00:34
Code
Stop Simulation
Send To
Slideswitch
Name 2
PMOS
PMOS
9V
SOWN
SOWN
A = 1, B = 0


Circuit design Surprising Waasa
Ask Gemini
tinkercad.com/things/24vRRQ5OI8E-surprising-waasa/editel?returnTo=https%3A%2F%2Fwww.tinkercad.com%2Fdashboard%2Fdesigns%2Fall
Swayam Central
AWS Academy Clou...
जयराम दरवेशपुरी - क...
Surprising Waasa
Circuits
Schematic
Components
Simulator time: 00:00:20
Code
Stop Simulation
Send To
PMOS
PMOS
9V
SOWN
SOWN
A = 1, B = 1